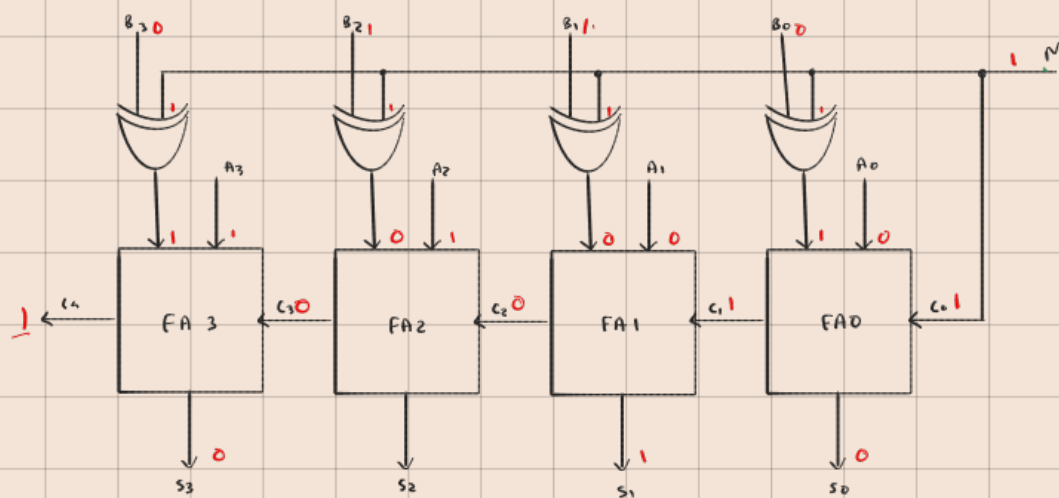


- Includes a xor gate with each Full Adder
- Uses a Control pin m
- $m = 0$ for adder, $m = 1$ for subtractor
- the xor gate complements the input and when $m = 1$ the first carry is also 1
- so basically the second number gets complemented and a 1 is added to it

$$\begin{array}{r} 1010 \\ 0101 \\ + \quad 1 \\ \hline 0110 \end{array}$$



$$\begin{array}{r} 1100 \quad A \\ + 0110 \quad B' \\ \hline 10010 \end{array}$$

1 0 1 1 0