

format for state table

P.S	inputs	N.S	outputs
-----	--------	-----	---------


Jk Flip Flop

State table

P.S	inputs		N.S
Q_n	T	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$Q_{n+1} = \bar{Q}_n T + Q_n \bar{K}$$

Q_n	Q_{n+1}	T	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

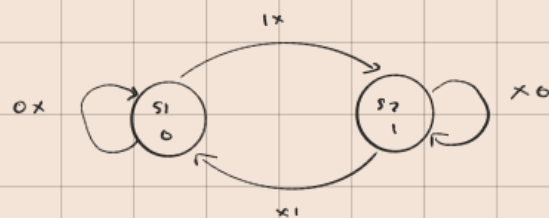

State Equation

$$L.H.S = R.H.S$$

$\swarrow$ $\searrow$
 Data/NS Present Input