
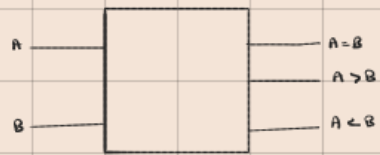


Comparator

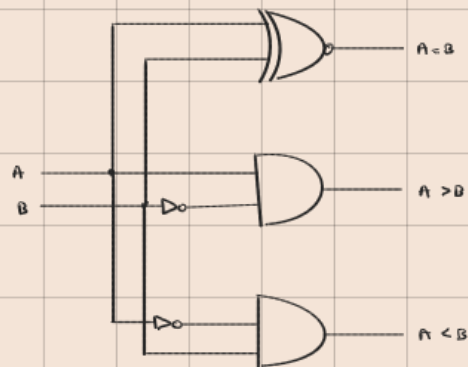

1-bit Comparator

A	B	A=B	A>B	A<B
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0




2-bit Comparator

A ₁	A ₀	B ₁	B ₀	A=B	A>B	A<B
0	0	0	0	1	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	1	0	0

$$A=B = (A_1 \oplus B_1) (A_0 \oplus B_0)$$

$$A>B = A_1 \bar{B}_1 (A_0 \oplus B_0) + A_0 \bar{B}_0$$
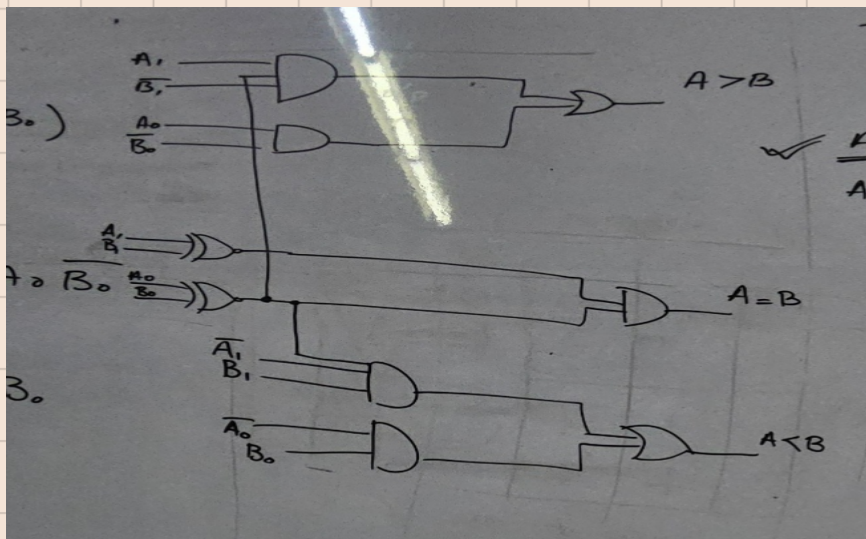
$$A<B = \bar{A}_1 \bar{B}_1 (A_0 \oplus B_0) + \bar{A}_0 B_0$$



4 bit

A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	A > B	A < B	A = B
0	0	0	0	0	0	0	0			
↓ 128	↓ 64	↓ 32	↓ 16	0	0	0	1			
				0	0	1	0			
1				0	0	1	1			
↓ 128				0						
				0						
				0						
				0						